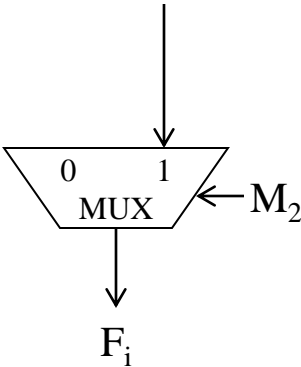


- Design a 4-bit ALU that implements the following set of operations with only the following components (assume 2's complement number representation, no need to implement overflow circuit)
 - 1-bit Full-Adders (FA)
 - 2-input AND/OR/XOR gates
 - Inverters
 - 2:1 MUX

M_2	M_1	M_0	Function Name	$F =$
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

M_2	M_1	M_0	Function Name	F =
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

M_2	M_1	M_0	Function Name	$F =$
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$




M_2	M_1	M_0	Function Name	F =
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

$A * 2 = \text{left-shift}$

e.g. $3 * 2 = \text{"011"} * 2 = \text{"110"} = 6$

$A / 2 = \text{right-shift}$

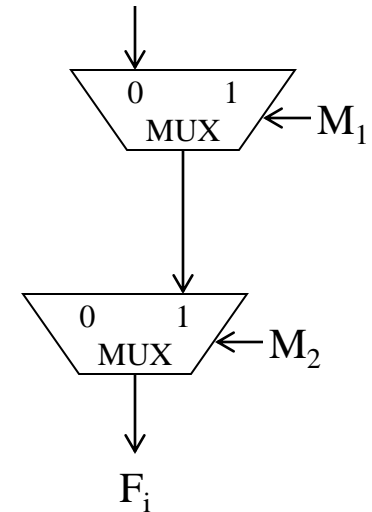e.g. $3 / 2 = \text{"011"} / 2 = \text{"001"} = 1$




M_2	M_1	M_0	Function Name	F =
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

$A * 2 = \text{left-shift}$


e.g. $3 * 2 = \text{"011"} * 2 = \text{"110"} = 6$

$A / 2 = \text{right-shift}$

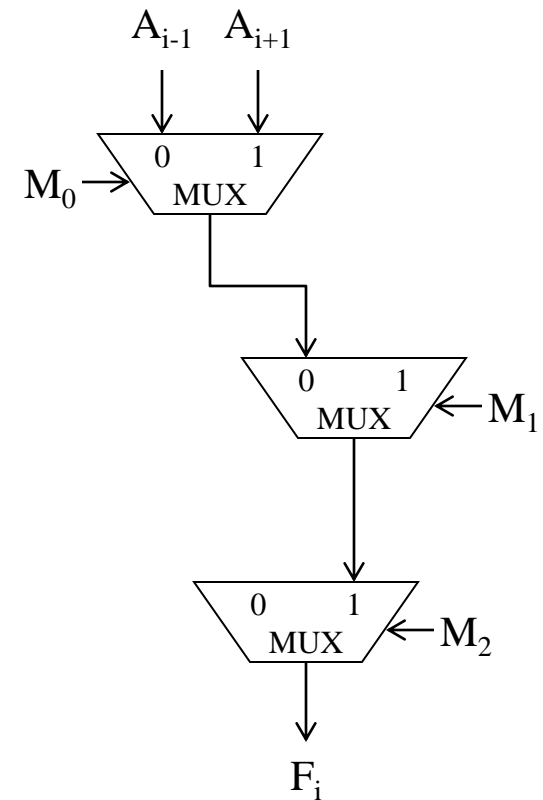
e.g. $3 / 2 = \text{"011"} / 2 = \text{"001"} = 1$





M_2	M_1	M_0	Function Name	$F =$
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

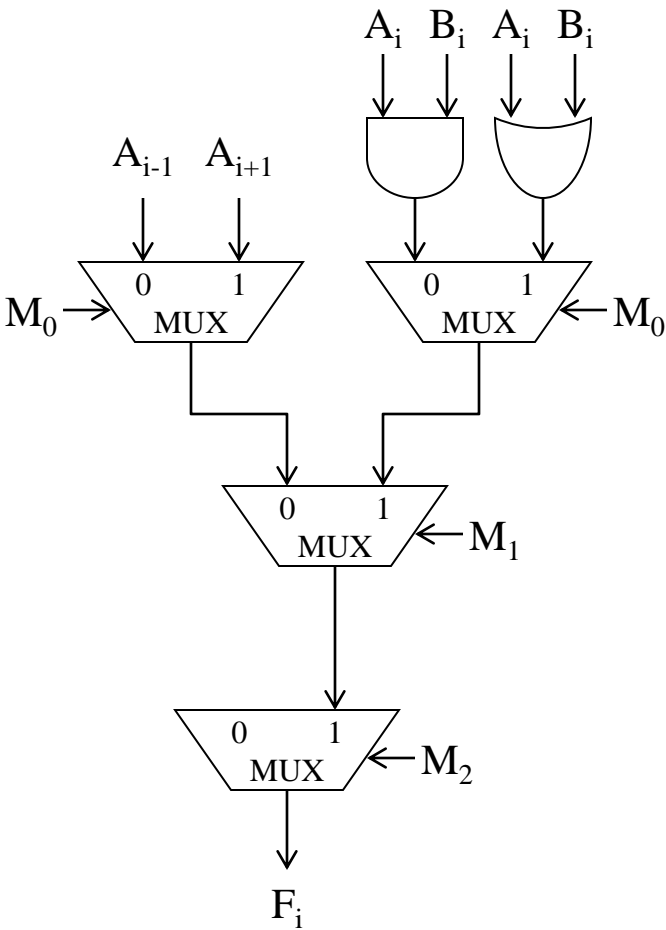


M_2	M_1	M_0	Function Name	F =
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

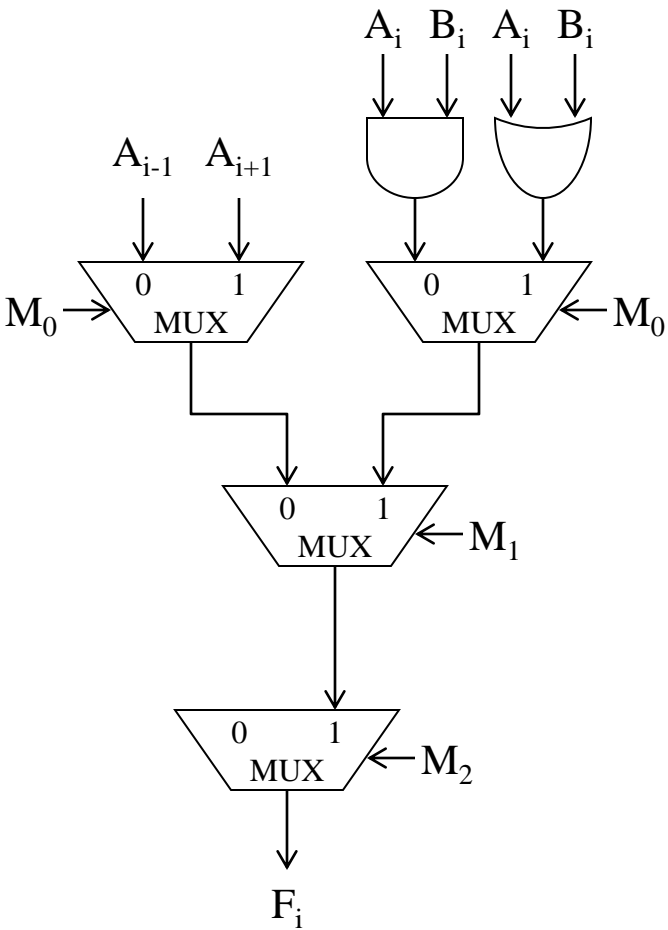


M_2	M_1	M_0	Function Name	F =
0	0	0	Add	$A + B$
0	0	1	Subtract	$A - B$
0	1	0	Increment	$A + 1$
0	1	1	Decrement	$A - 1$
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1	1	0	Bitwise-AND	$A \text{ AND } B$
1	1	1	Bitwise-OR	$A \text{ OR } B$

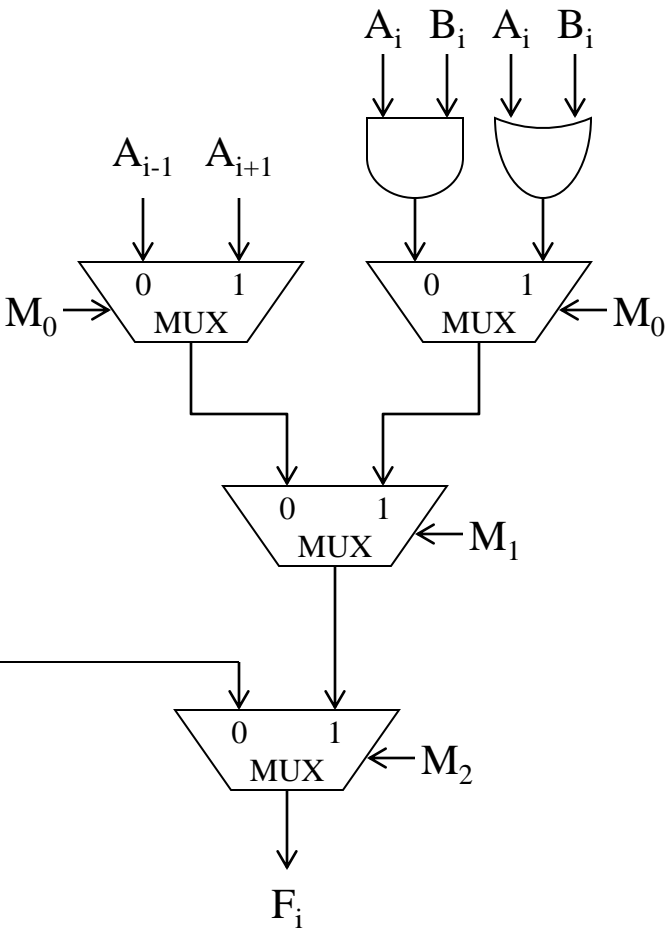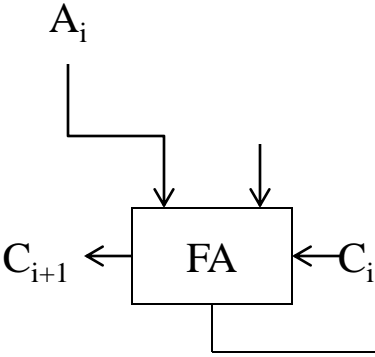


M_2	M_1	M_0	Function Name	$F =$		C_0
0	0	0	Add	$A + B$	B_i	0
0	0	1	Subtract	$A - B$	$\text{NOT}(B_i)$	1
0	1	0	Increment	$A + 1$	“0”	1
0	1	1	Decrement	$A - 1$	“1”	0
1	0	0	Multiply by 2	$A * 2$		
1	0	1	Divide by 2	$A / 2$		
1	1	0	Bitwise-AND	$A \text{ AND } B$		
1	1	1	Bitwise-OR	$A \text{ OR } B$		

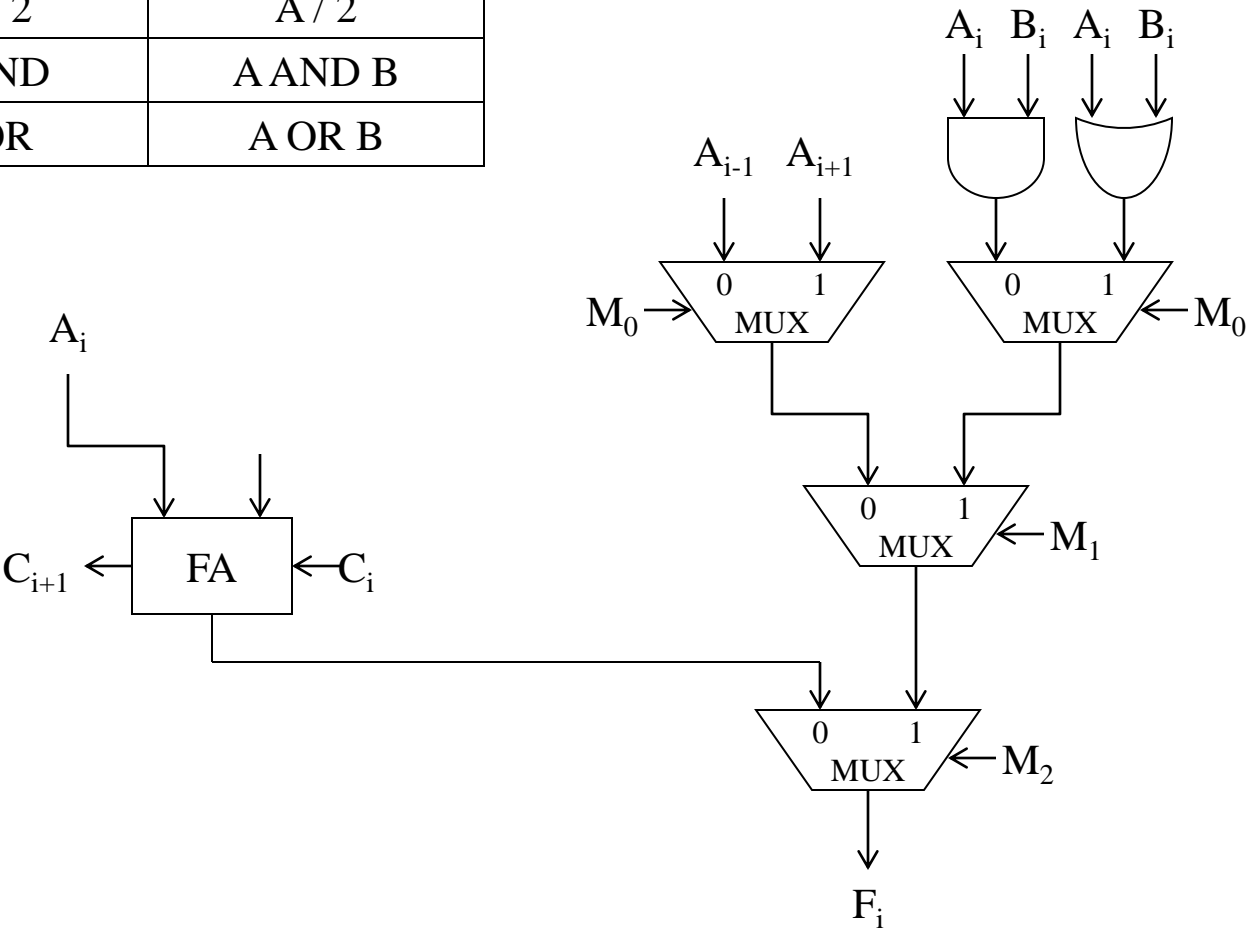


M_2	M_1	M_0	Function Name	$F =$		C_0
0	0	0	Add	$A + B$	B_i	0
0	0	1	Subtract	$A - B$	$\text{NOT}(B_i)$	1
0	1	0	Increment	$A + 1$	"0"	1
0	1	1	Decrement	$A - 1$	"1"	0
1	0	0	Multiply by 2	$A * 2$		
1	0	1	Divide by 2	$A / 2$		
1	1	0	Bitwise-AND	$A \text{ AND } B$		
1	1	1	Bitwise-OR	$A \text{ OR } B$		

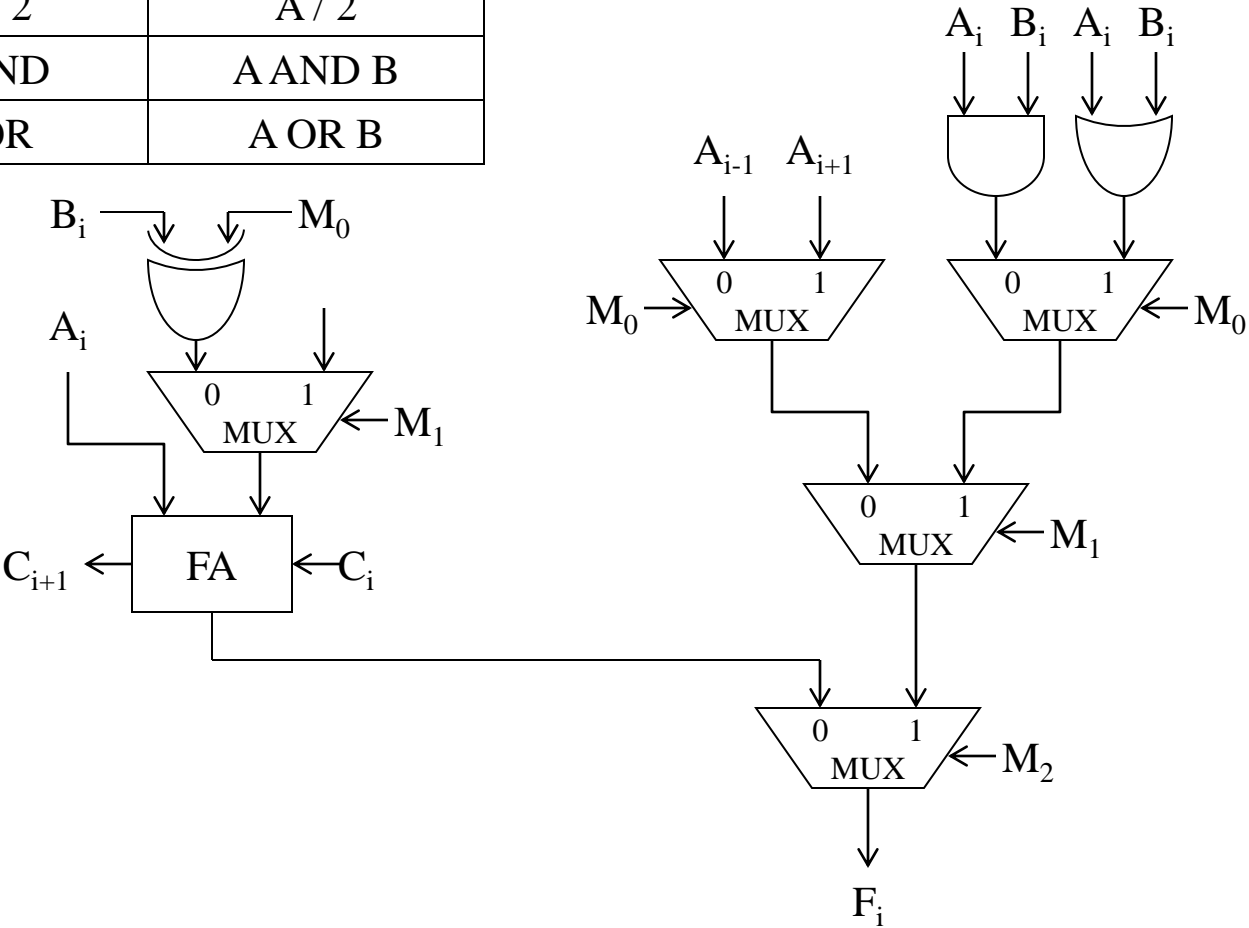



M_2	M_1	M_0	Function Name	$F =$		C_0
0	0	0	Add	$A + B$	B_i	0
0	0	1	Subtract	$A - B$	$\text{NOT}(B_i)$	1
0	1	0	Increment	$A + 1$	"0"	1
0	1	1	Decrement	$A - 1$	"1"	0
1	0	0	Multiply by 2	$A * 2$		
1	0	1	Divide by 2	$A / 2$		
1	1	0	Bitwise-AND	$A \text{ AND } B$		
1	1	1	Bitwise-OR	$A \text{ OR } B$		

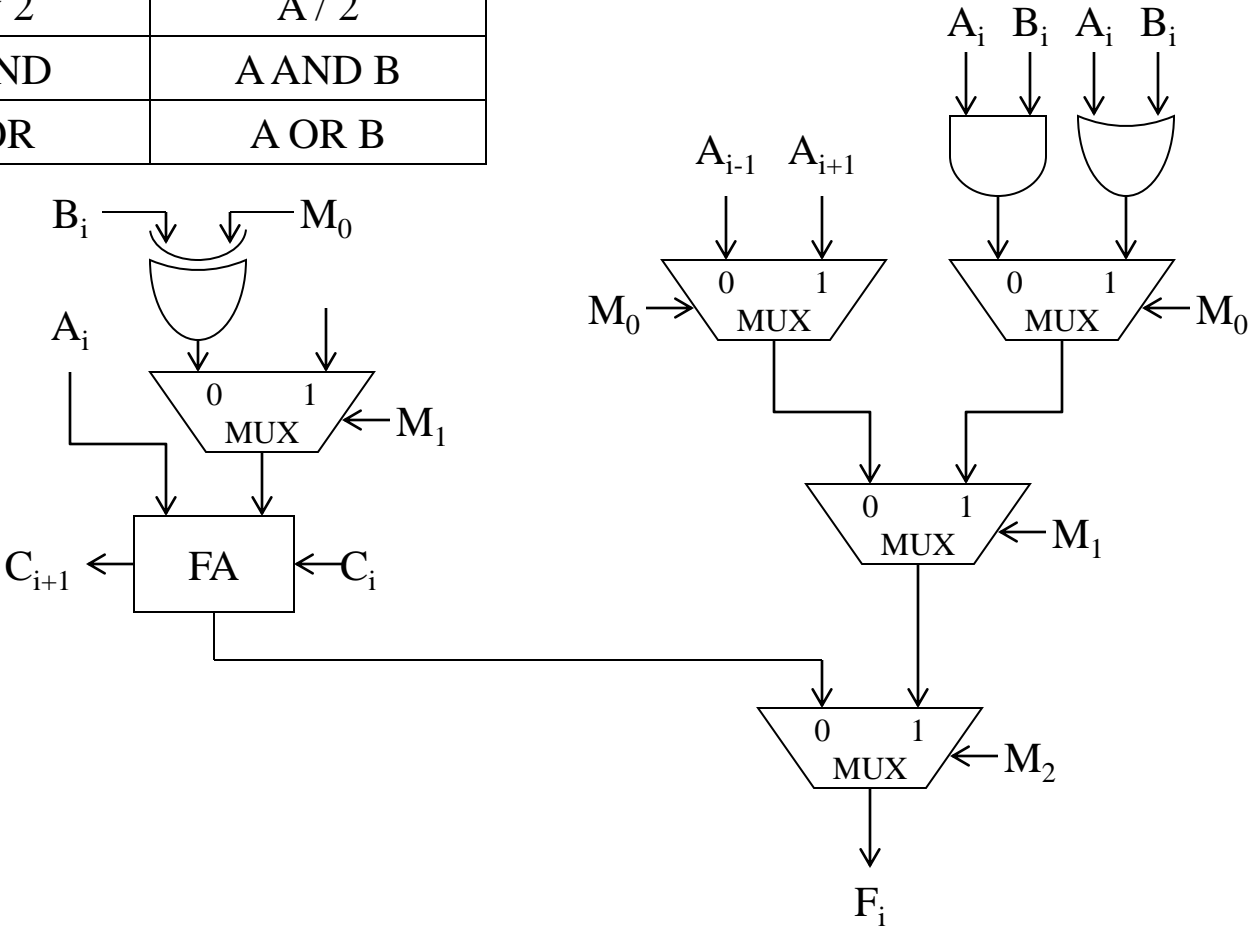



M_2	M_1	M_0	Function Name	$F =$		C_0
0	0	0	Add	$A + B$	B_i	0
0	0	1	Subtract	$A - B$	$\text{NOT}(B_i)$	1
0	1	0	Increment	$A + 1$	"0"	1
0	1	1	Decrement	$A - 1$	"1"	0
1	0	0	Multiply by 2	$A * 2$		
1	0	1	Divide by 2	$A / 2$		
1	1	0	Bitwise-AND	$A \text{ AND } B$		
1	1	1	Bitwise-OR	$A \text{ OR } B$		

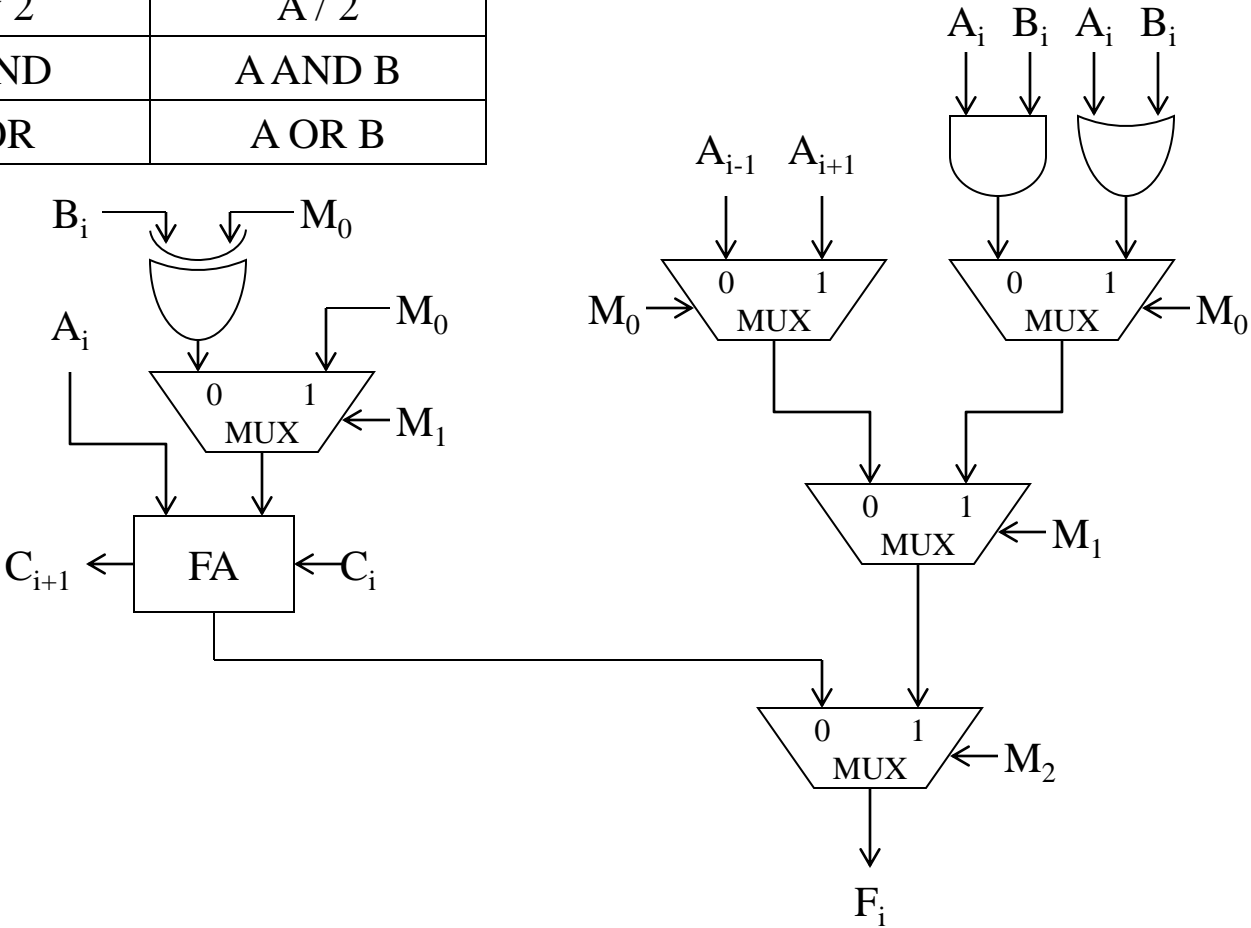




M_2	M_1	M_0	Function Name	$F =$		C_0
0	0	0	Add	$A + B$	B_i	0
0	0	1	Subtract	$A - B$	$\text{NOT}(B_i)$	1
0	1	0	Increment	$A + 1$	"0"	1
0	1	1	Decrement	$A - 1$	"1"	0
1	0	0	Multiply by 2	$A * 2$		
1	0	1	Divide by 2	$A / 2$		
1	1	0	Bitwise-AND	$A \text{ AND } B$		
1	1	1	Bitwise-OR	$A \text{ OR } B$		

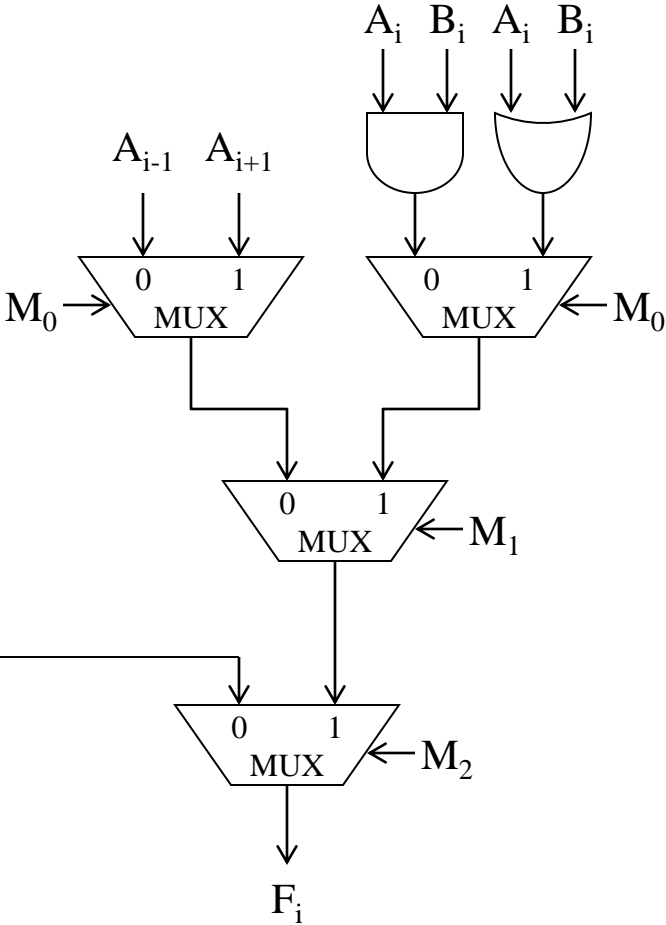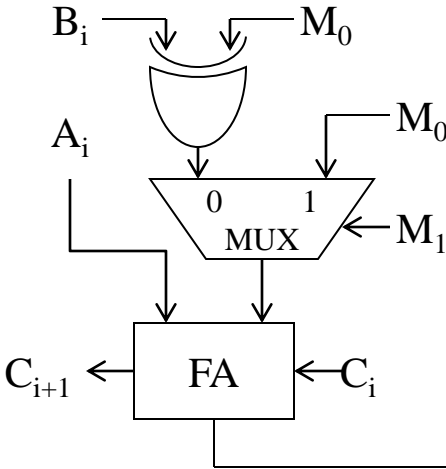



M_2	M_1	M_0	Function Name	$F =$		C_0
0	0	0	Add	$A + B$	B_i	0
0	0	1	Subtract	$A - B$	$\text{NOT}(B_i)$	1
0	1	0	Increment	$A + 1$	"0"	1
0	1	1	Decrement	$A - 1$	"1"	0
1	0	0	Multiply by 2	$A * 2$		
1	0	1	Divide by 2	$A / 2$		
1	1	0	Bitwise-AND	$A \text{ AND } B$		
1	1	1	Bitwise-OR	$A \text{ OR } B$		

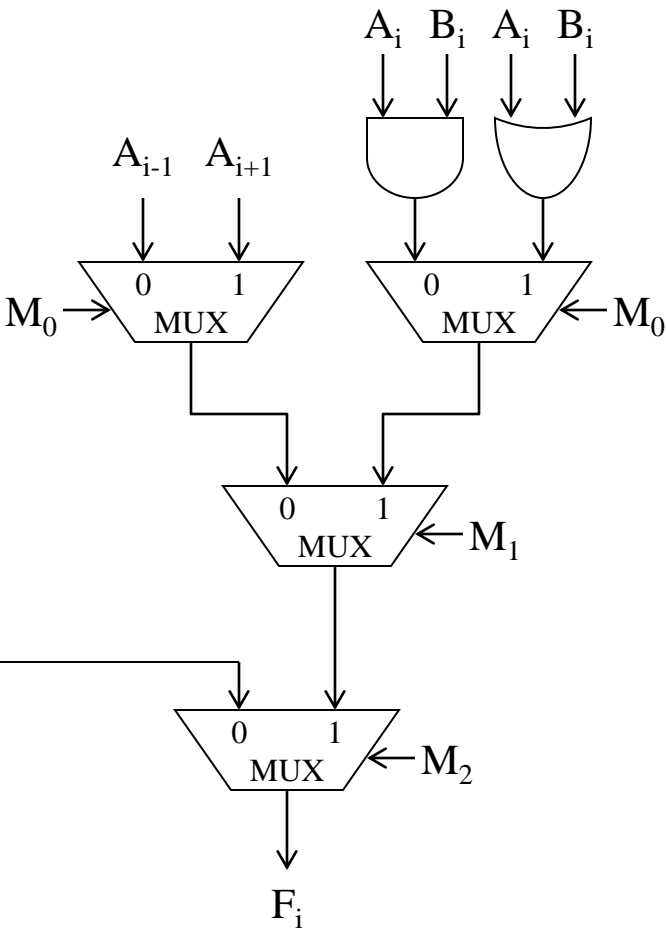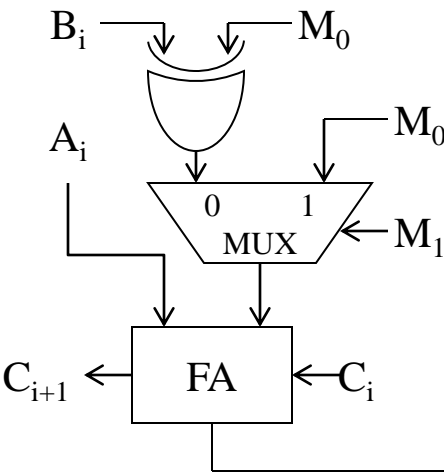

M_2	M_1	M_0	Function Name	$F =$
0				
0				
0				
0				
1				
1				
1				
1				

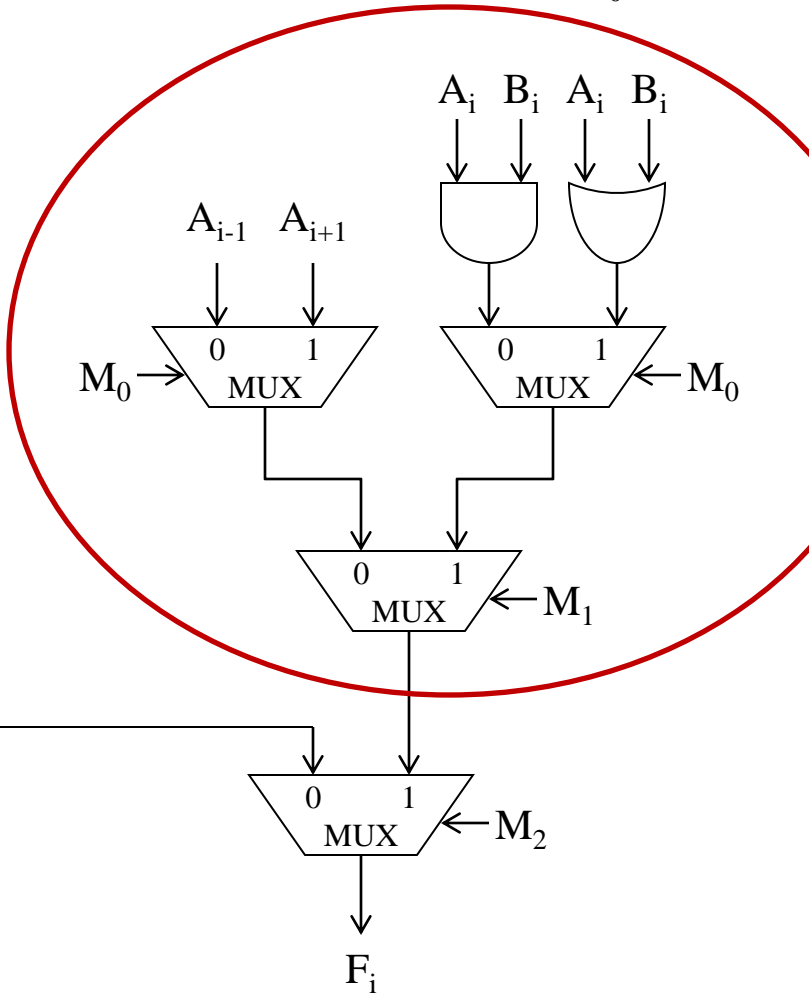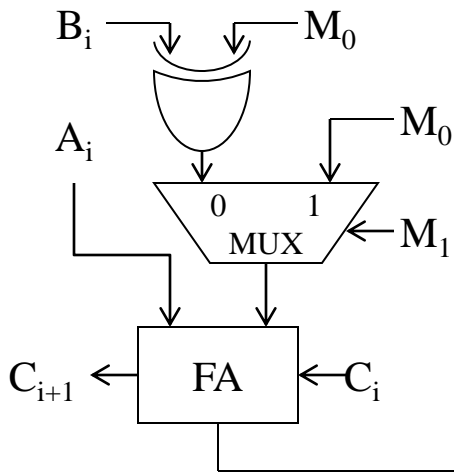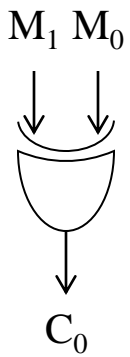

M ₂	M ₁	M ₀	Function Name	F =
0				
0				
0				
0				
1				
1				
1	1	0	Bitwise-AND	A AND B
1	1	1	Bitwise-OR	A OR B

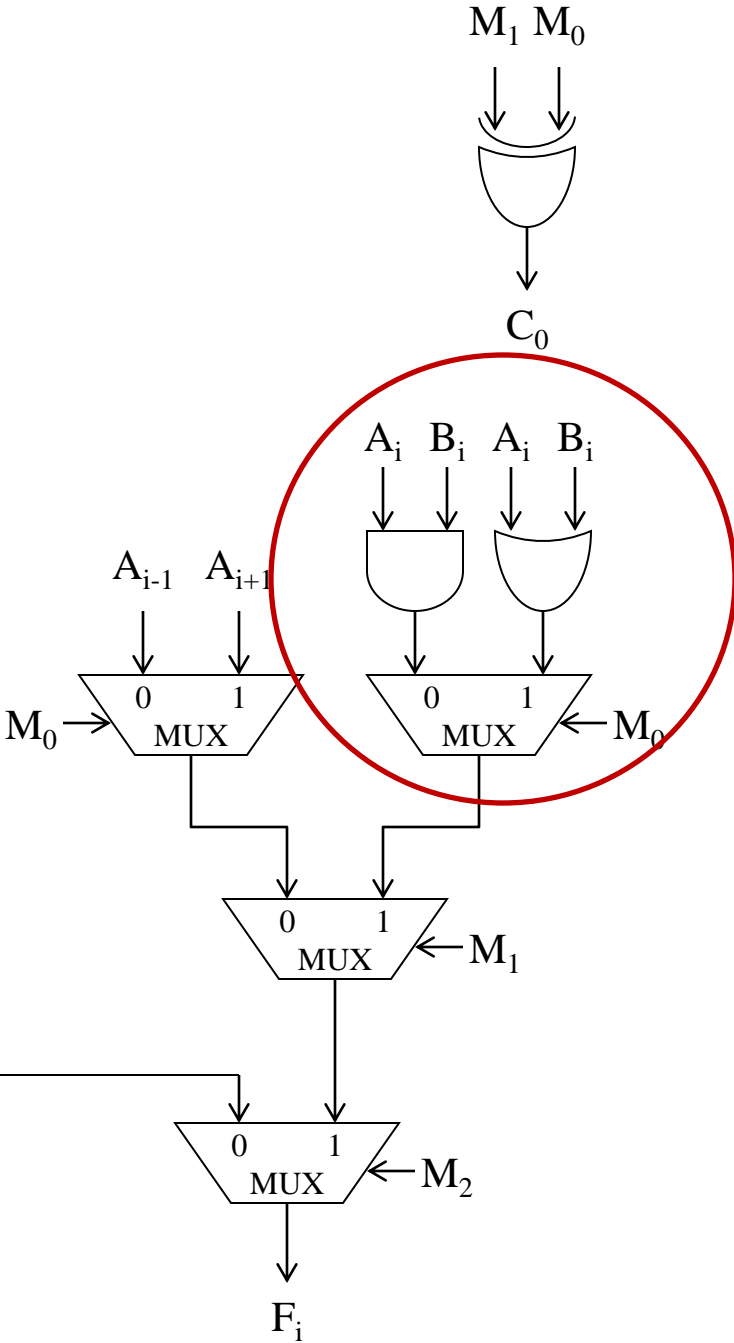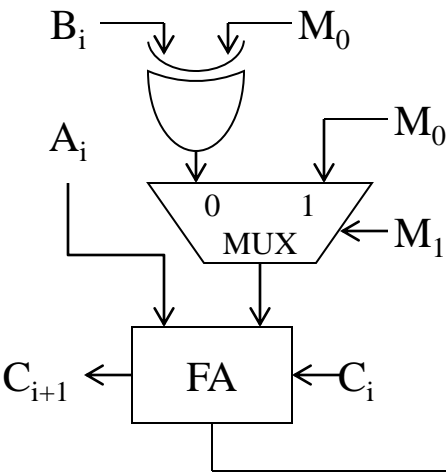

M_2	M_1	M_0	Function Name	$F =$
0				
0				
0				
0				
1	0	0	Multiply by 2	$A * 2$
1	0	1	Divide by 2	$A / 2$
1				
1				

